

ELEC 341 – Graded Assignments

# Assignment A3 Mechanical Circuits

## 100 Marks

### Required Files

Available on Canvas

- **e341-a3.pdf**
- **a3Submit.p**
- **e341-APE.pdf**

*Assignment description (this document)*

*Grading script (**LATEST** version)*

*Instructions for submitting graded work (for reference)*

### Topics

Electro-Mechanical Equivalents

- mechanical circuit analysis


Motor Model

- mixed mode systems

Power & Energy

- conservation of energy

Figure 1

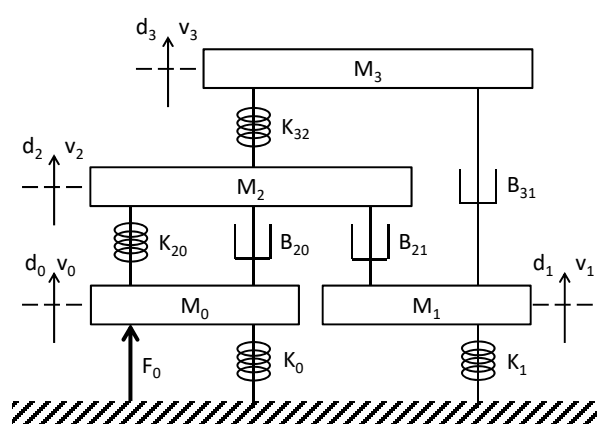

When an **Applied Force** puts a spring **K** in **Compression**, it reacts with a **Separating Force**.

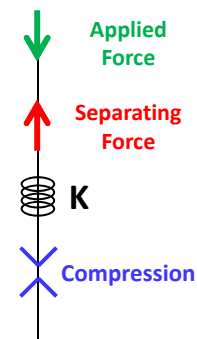


Figure 2

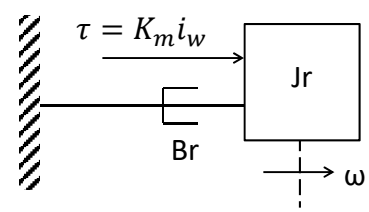
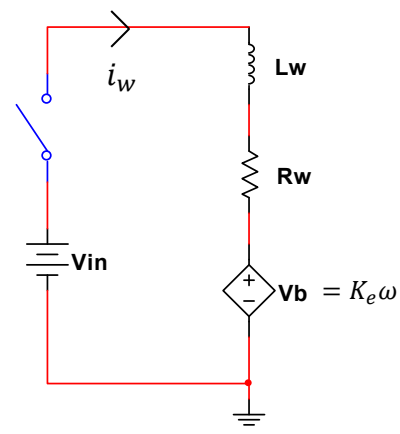


Figure 1 Parameters			Figure 2 Parameters		
Parameter	Value	Physical Units	Parameter	Value	Physical Units
M <sub>0</sub>	#A / 5	Kg	R <sub>w</sub>	#A / 3	Ω
M <sub>1</sub>	#B / 10	Kg	L <sub>w</sub>	#B	mH
M <sub>2</sub>	#C / 10	Kg			
M <sub>3</sub>	#D / 5	Kg	J <sub>r</sub>	#C / 10	m-Nms <sup>2</sup>
			B <sub>r</sub>	#D + #E	m-Nms
B <sub>20</sub>	#E / 2	Ns/m			
B <sub>21</sub>	#F / 3	Ns/m	K <sub>e</sub>	#G x 50	m-Vs
B <sub>31</sub>	#G / 4	Ns/m	K <sub>m</sub>	#G x 50	m-Nm/A
K <sub>0</sub>	#A	N/m			
K <sub>1</sub>	#B	N/m			
K <sub>20</sub>	#C	N/m			
K <sub>32</sub>	#D / 3	N/m			

Transform the mechanical circuit in **Figure 1** into its electrical equivalent.  
Use nodal analysis to solve the circuit.  
Find the transfer function:  $G_{d1} = d_1/F_0$   
Find the transfer function:  $G_{d3} = d_3/F_0$

**1. 20 mark(s) Distance Gains**

- Q1.Gd1 (m/N) LTI
- Q1.Gd3 (m/N) LTI

Find the transfer function:  $G_{f1} = f_{k1}/F_0$   $f_{k1}$  is separating force in spring  $K_1$   
Find the transfer function:  $G_{f32} = f_{k32}/F_0$   $f_{k32}$  is separating force in spring  $K_{32}$

**2. 20 mark(s) Force Gains**

- Q2.Gf1 (N/N) LTI
- Q2.Gf32 (N/N) LTI

**COW:** Plot the Step Response of each transfer function.  
When the step is first applied, does the mass move in the right direction ???  
After a long time, does the FV make sense ???  
Do not confuse Distance with Velocity.

A model of an electric motor is shown in **Figure 2**.  
The motor model integrates electrical and mechanical systems with dependent sources.  
Rotor torque  $\tau$  depends on winding current  $i_w$ , and winding back-EMF (voltage)  $v_b$  depends on rotor speed  $\omega$ .  
Convert the mechanical system into its electrical equivalent, and combine the two systems.  
Use nodal analysis to solve the circuit.  
Find the transfer function:  $G_i = i_w/V_{in}$   
**3. 20 mark(s) Current Gain**  
• Q3.Gi (A/V) LTI  
  
Find the transfer function:  $G_w = \omega/V_{in}$   
**4. 20 mark(s) Speed Gain**  
• Q4.Gw (rad/Vs) LTI  
  
**COW:** Plot a 1V Step Response.  
Do the Peak & Final values seem reasonable ???  
Are they the same ??? Should they be ???

Use  $G_i$  and  $G_w$  to find current and speed for a **1V** unit step input.  
Find the power dissipated by the resistor  $R_w$  and the bearings (damper  $B_r$ ).  
Use the electrical analogy to determine mechanical power dissipation.  
Estimate the total **energy** dissipated after **50 ms**. Use **1 ms** time increments.  
The area under a curve can be approximated by summing the parts (as shown).  
Find the total energy dissipated  $E_d$  after **50 ms**.  
Find the energy stored in the inductor  $L_w$  and inertia  $J_r$  after **50 ms**.  
Find the total energy stored  $E_s$  after **50 ms**.  
Find the total energy provided  $E_p$  by the source  $V_{in}$  after **50 ms**.

- 5. 20 mark(s) Energy**
- Q5.Ed (J) Scalar
  - Q5.Es (J) Scalar
  - Q5.Ep (J) Scalar

**COW:** Does  $E_p = E_d + E_s$  ???  
“Conservation of Energy” must always hold.

